

BLACK1.TXT

The TRUTH about Black Boxing !... By Fabulist /// ENIGMA /// 1992

THE INFORMATION IS FOR THE GREEK TELEPHONE NETWORK
BUT THEY CAN BE EASILY CONVERTED FOR USING THEM IN OTHER COUNTRIES

Black Box is a little device which is beeing used by phone freaks (phreaks!) so that the one who calls you,won't pay anything.That's only FOR 1 MINUTE in MOST places,but NOT everywhere.In northen Greece ,as far as i know, 1 minute was firstly used in 1992...Pity...The way the boxy works is simple : it makes the telephone center beleive that your phone is still ringing and that's why NO charge is made! ;-)

NOTICE : PLEASE DON'T call youself a "phreak" before you have managed to BUILD at LEAST a WORKING Black BOX!!

Materials Needed

- 1st) A phone device
- 2nd) A 2.7K Ohm resistor 1/2 Watt (colors : red purple red ,which means 2 + 7 + the numbers of zeros at the end ... 2+7+00 Ohm.You will probably find a silver or gold color which represents the accuracy of the resistor. Not really needed but you must put it to the right side and read the colors from the left...)
- 3rd) A little switch with 3 poles (SPDT?)
- 4rth) A LED (Light Emitting Diode)
- 5th) A soldering iron
- 6th) A screw driver

Construction

Choose a small and portable phone device and make all your telephone lines in your house easy to modify.This will help you to use many boxes and/or normal phones without fass.Just plug and use!

Now open the back of the phone.You will probably find a mess of wires and electronic componends.Ignore everything and look for a GREEN (tip) and a RED (ring) wire,which are coming in from the inlet.The colors may be different (usually they arent) so be carefull.Leave GREEN as it is and unsolder the RED one...

1st SHEMATIC (Without a switch.The Box is always on.)

ñAAAAAAAAAAAAAGREENAAAAAAAAAAAAñ

ñAAAAAAAREDAARESTORAAAALEDAAAñ

2nd SCHEMATIC (With a switch.LED on BOX on)

