

U

TELEPHONE MOD TIPS  
BY THE LEFTIST

In this file, im not gonna waste a bunch of time with pretty borders etc.  
instead, im gonna spend that time giving you more ways to make your fone trippy

1> music on hold. Does just what the name implies.

you will need-

D1 light emitting diode

D2 1N914, or any silicon diode.

R1 1200-ohm resistor


R2 820-ohm resistor

T1 1000-to 8 -ohm transformer

SCR RS 1020(radio shack)

SW spst momentary contact pushbuton.

THE CIRCUIT

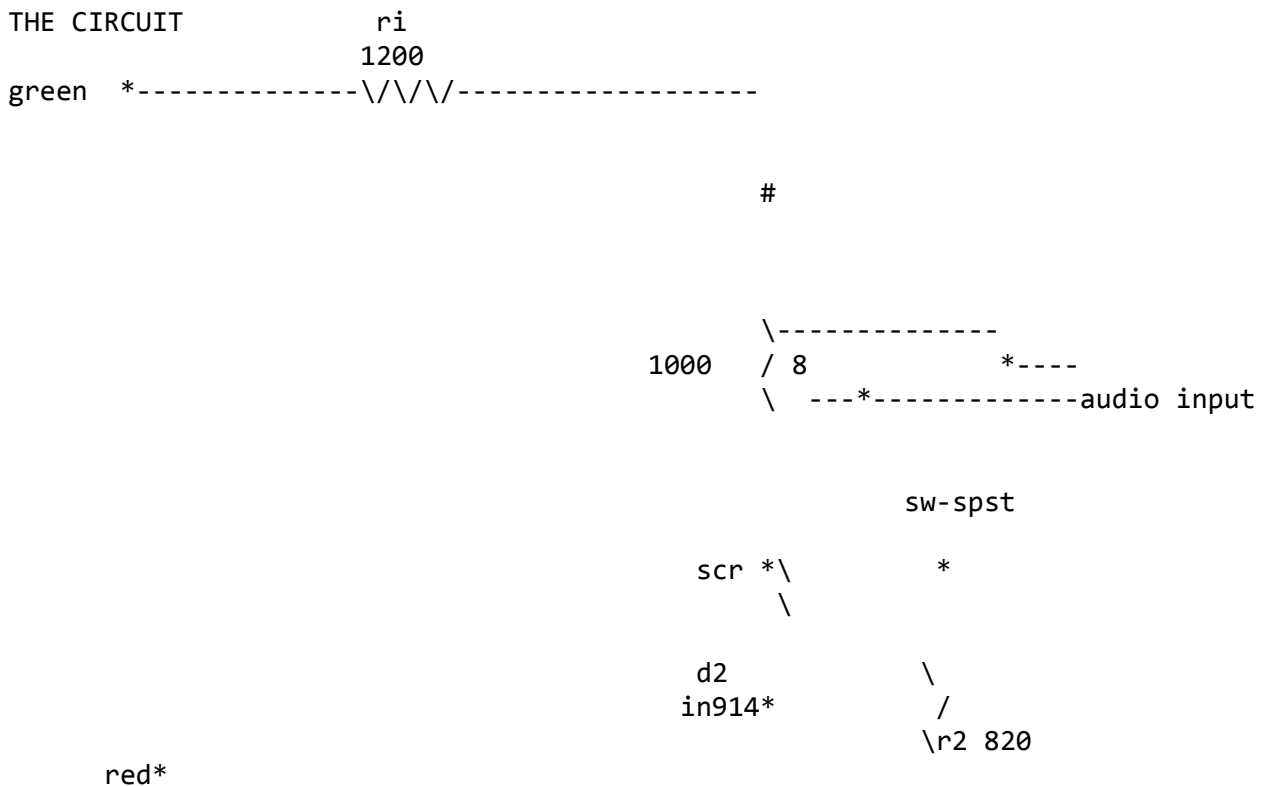

you can get all the parts for a very small amount of money.

## FONEMODS.txt

This project requires you a direct connect to the phone line.  
Note, that some fone companies object to to customers<thats you>  
making such connections for fear of that they might introduce large amounts  
of high voltage to the lines. this proj. does not createhigh voltage,  
but i wouldnt go callin them and askin if it's ok.  
more in later files

THE LEFTIST ^\*^

[illegible]

Ever been in bed with your woman, the phone rings, and you get pissed? well, heres a sure fire way to end your sexual problems on this point. This little gadget will flash rapidly when the phone rings, but wont let the bell ring.

## Parts list

D1 1n914, or any silicon diode

D2 LED of any type

R 10,000-ohm, 1/2-watt resistor

SW spdt switch

the circuit

```

                                10 k      in 914
yellow /sw-----/\/\/\-----
/-----*/
          * normal                      d2    led
<-----
\-----

```

Downloaded From P-80 Systems 304-744-2253