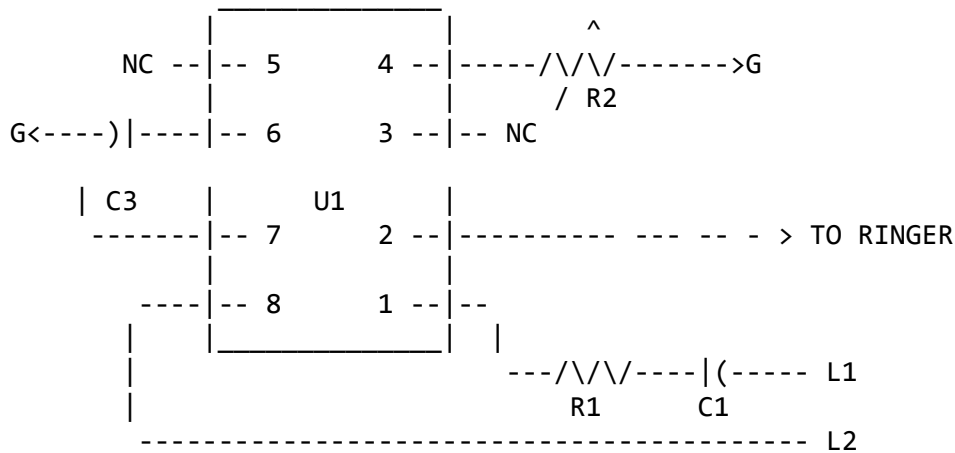



OLIVEBOX.TXT

```
(>.....<)
(>.....<)
(>      Olive Box Plans      <)
(>.....<)
(>.....<)
```


This is a relatively new box, and all it basically does is serve as a phone ringer. You have two choices for ringers, a piezoelectric transducer (ringer), or a standard 8 ohm speaker. The speaker has a more pleasant tone to it, but either will do fine. This circuit can also be used in conjunction with a rust box to control an external something or other when the phone rings. Just connect the 8 ohm speaker output to the inputs on the rust box, and control the pot to tune it to light the light (which can be replaced by a relay for external controlling) when the phone rings.



a. Main ringer TTL circuit

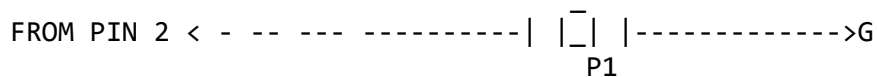[illegible]

b. Piezoelectric transducer

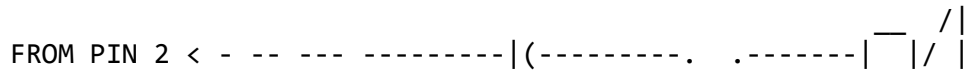[illegible]

Parts List

- Shift Rate:
-
-

$$SR = \frac{1}{(DSR(1/f_1) + DSR(1/f_2))} = \frac{1}{\frac{128}{1714} + \frac{128}{1500}} = 6.25 \text{ Hz}$$

```
(>:.....r:2:.....:<)<
(>  Another fine box plan by:      <)<
(>                                  <)<
(>          A R N O L D !           <)<
(>                                  <)<
(>  Sysop: HHAЕ East                <)<
(>:.....:<)<
(>  Hobbit Hole Network:            <)<
(>                                  <)<
```

OLIVEBOX.TXT

```
(> Hobbit Hole AE Line Network HQ ..... (609)-429-3641 <)  
>      3 drives... No password... 300b only <  
> <  
> Hobbit Hole AE Line North Branch ... (215)-271-0778 <  
>      x drives... No password... 300/1200b <  
> <  
> Hobbit Hole AE Line East Branch .... (201)-271-0256 <  
>  4 drives... No password... 300b, 1200 AFTER logon <  
> <  
> Sirius Cybernetics 60 Megs ..... (808)-528-2436 <  
> one of the largest phreak boards in the country! <  
> <  
>:.....<
```

DOWNLOADED FROM P-80 SYSTEMS.....