

From: bill

Subject: Phone line as SW antenna


[Last modified 18-Feb-93]

This article describes how to use a phone line as a shortwave antenna. Performance will vary depending on the kind of line you have. Overhead lines make fairly good antennas, while underground lines generally don't.

A highpass filter is used to remove signals below the shortwave bands. This improves rejection from local AM stations. In addition, a lowpass filter can be used to reject interference from FM stations.

The original credit for the highpass and lowpass filters goes to Paul Blumstein and John Shalamskas, respectively. I have included edited versions of their articles below.

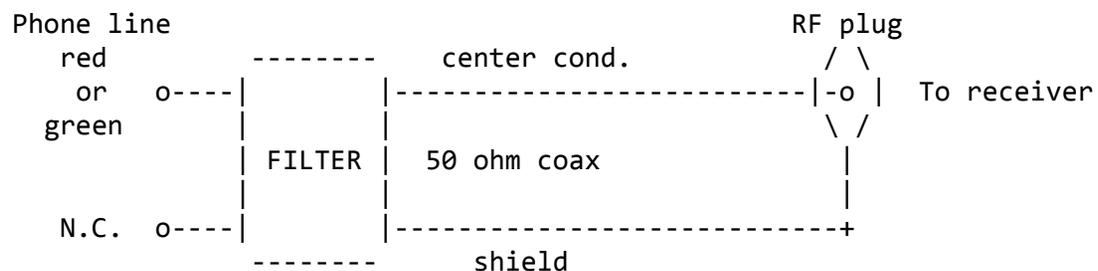The filter(s) should be connected to the phone line in this manner:



Phone\_Line\_As\_Sw\_Antenna\_2004.txt

N.C. = no connect. Alternatively, you could connect this to a ground. I tried the phone line ground (yellow wire) and it worked more poorly than no ground at all. I haven't tried any other ground, because that would defeat the purpose of a portable antenna.

If the highpass filter is used, all phone line voltages, including ringing, are eliminated and thus will not harm the receiver. I should also mention that this filter works very well with random wire antennas.

Someone who wrote asked about lightning protection. I haven't thought much about this because thunderstorms are rare in my area. However, I believe most phone lines have lightning arrestors on them where they enter the house. Anyway, my suggestion would be to unplug the antenna when not in use if you experience frequent thunderstorms.

Okay, here are the articles on the filter designs:


Date: 09 Jan 91 00:54:08 GMT  
From: paul  
Subject: BC Band Hi-Pass Filter

The following ascii-schematic diagram is a high pass filter that will filter out Broadcast Band (MW) stations. I found it a great boon to my shortwave listening since local MW stations overload my ATS-803A front end & appear in SW, especially with a long antenna.

If you remember my antenna saga, I went from 50 feet to 150 feet & had overload problems causing me to cut back to 50 feet. (Even at 50 feet, I still have some MW interference). I took the advice of Gary Coffman and looked up filters in the ARRL Handbook. With the filter in place, I intend to try to increase my antenna length again.

Phone\_Line\_As\_Sw\_Antenna\_2004.txt

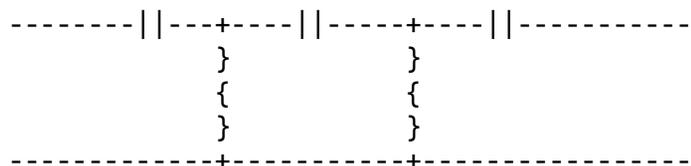Anywho, here is the filter, for interested parties.



The outer capacitors are 1500 pf ceramic disks.  
The inner capacitor is 820 pf ceramic disk.  
The squiggly things are coils (two total). Each one is 2.7 uh.  
(a close value will do).

Date: 12 Jan 91 00:44:25 GMT  
From: bill@videovax.tv.tek.com (William K. McFadden)  
Subject: Re: BC Band Hi-Pass Filter

I built the filter that Paul Blumstein posted recently and measured it on a gain-phase analyzer. Here are its characteristics:

100 KHz -120dB  
500 KHz -68dB  
1000 KHz -38dB  
1600 KHz -15dB  
2100 KHz -3dB

The source and load impedances were 50 ohms. Because the filter has five elements, the attenuation is 30dB per octave. The measurements confirmed this.

Phone\_Line\_As\_Sw\_Antenna\_2004.txt

This filter seems to be a pretty good compromise between interference attenuation and passband response. There is very little attenuation in the 120m band and above. It could use a little more attenuation at the upper end of MW, which could be done with more stages or a higher cutoff frequency. Alternatively, you could build two of these filters and put them in series. (Since two 1500pF capacitors in series are really 750pF, you could eliminate one cap.)

Just for fun, I decided to put 470 ohms in series with the input to see how the filter performs with an antenna mismatch. The characteristics were:

100 KHz -105dB  
500 KHz -60dB  
1000 KHz -35dB  
1600 KHz -15dB  
2300 KHz -3dB


These figures are normalized to the passband response of -15dB, which is due to the impedance mismatch between the source and load and would have been there without the filter. Hence, the filter works almost as well in spite of the mismatch, which is good news to those who use longwire antennas.

Date: 22 Apr 92 08:59:33 GMT  
From: johns  
Subject: Construction of filters for SW reception

Several people have asked for construction details of the filters I built for my DX-440.

The high-pass filter helped some, but in my location the VHF/UHF

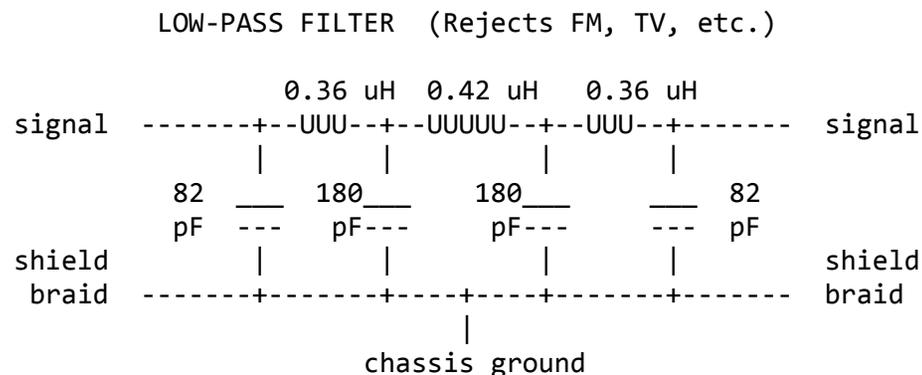broadcasters are also causing problems. So, I dug out the ARRL handbook and chose a 7-element Chebyshev low-pass design that is -3 dB at 35 MHz, -20 dB at 43 MHz, and -50 dB at 64 MHz (all calculated; it works well in practice!)



I had to do a little more improvising at this point. I used .33 uH instead of .36, and .66 uH instead of .42, but it works fine.

The 5-lug terminal strips were perfect for these circuits, since there are 4 lugs plus a grounded lug. All "ground" connections go to the lug that is mounted to the chassis, and the other 4 lugs are used for each of the connections on the signal line. One terminal strip is used per filter. Since both filters were necessary to clean up the hash, I am going to put them both into one box when I get the time.

The proper way to connect them is in series, i.e.



There is no difference between ends. They are "bilateral"  
which means you can't possibly hook them up backwards.  
(In the above schematics, left and right ends are interchangeable.)

#### COIL WINDING

If you can't locate the coils, you can make them yourself using this  
formula:

$$L = 0.2 * B^2 * N^2 / (3B + 9A + 10C)$$

L is inductance, in uH

A is length of coil, in inches

B is mean diameter of coil, in inches

C is the diameter of the wire, in inches

N is the number of turns

For small wire, you can assume  $C = 0$ .